
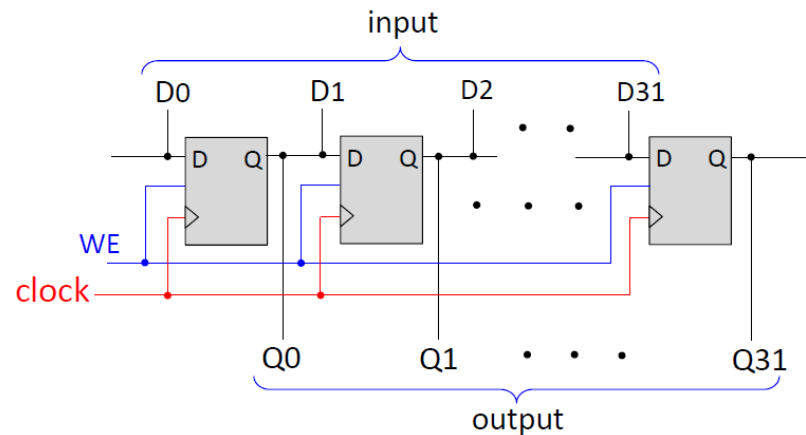
 


SC3050
Advanced Computer Architecture

Lab 2 briefing

College of Computing and Data Science
Nanyang Technological University

Register file

 

Keep in mind

- Synthesis by keeping DSIZE=64
 - Need to change the NREG from 4 to 64
 - When we change the NREG (no of registers) the address size also need to be changed.
 - Hence when NREG=4, ASIZE(address size)=2
 - NREG=8, ASIZE(address size)=3
 - NREG= 2^n , ASIZE(address size)=n
- Synthesis by keeping NREG=32
 - Need to change the DSIZE from 4 to 64
 - When we change the DSIZE the address size doesn't need to be changed.
- The number of LUTs is directly available in design summary, the delay here is the minimum clock period and not the combinational delay as this is a sequential circuit

datapath simplified- R format

opcode	Rm	shamt	Rn	Rd
31	21 20	16 15	10 9	5 4

Examples:

1. ADD X5, X4, X3 (meaning: $X5 \leftarrow (X4 + X3)$). The machine format is given below.


000000000000	00011	000000	00100	00101
31	21 20	16 15	10 9	5 4

2. XOR X8, X9, X10 (meaning: $X8 \leftarrow X9 \text{ (XOR) } X10$):


000000000011	01010	000000	01001	01000
31	21 20	16 15	10 9	5 4

R – register type instructions(ADD, SUB, AND, XOR, and ORR)

Datapath for R type instructions

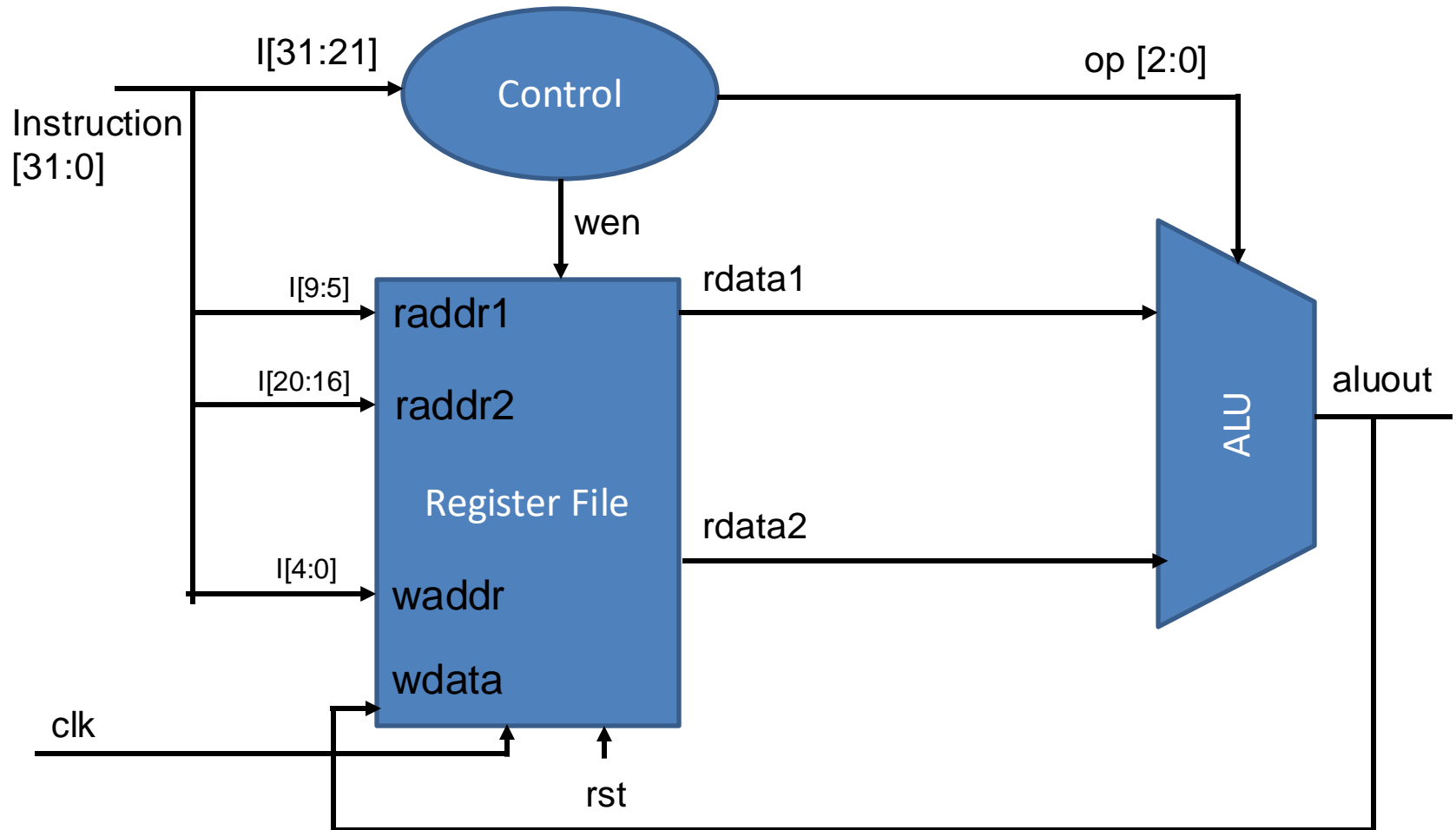

Module instantiation- example

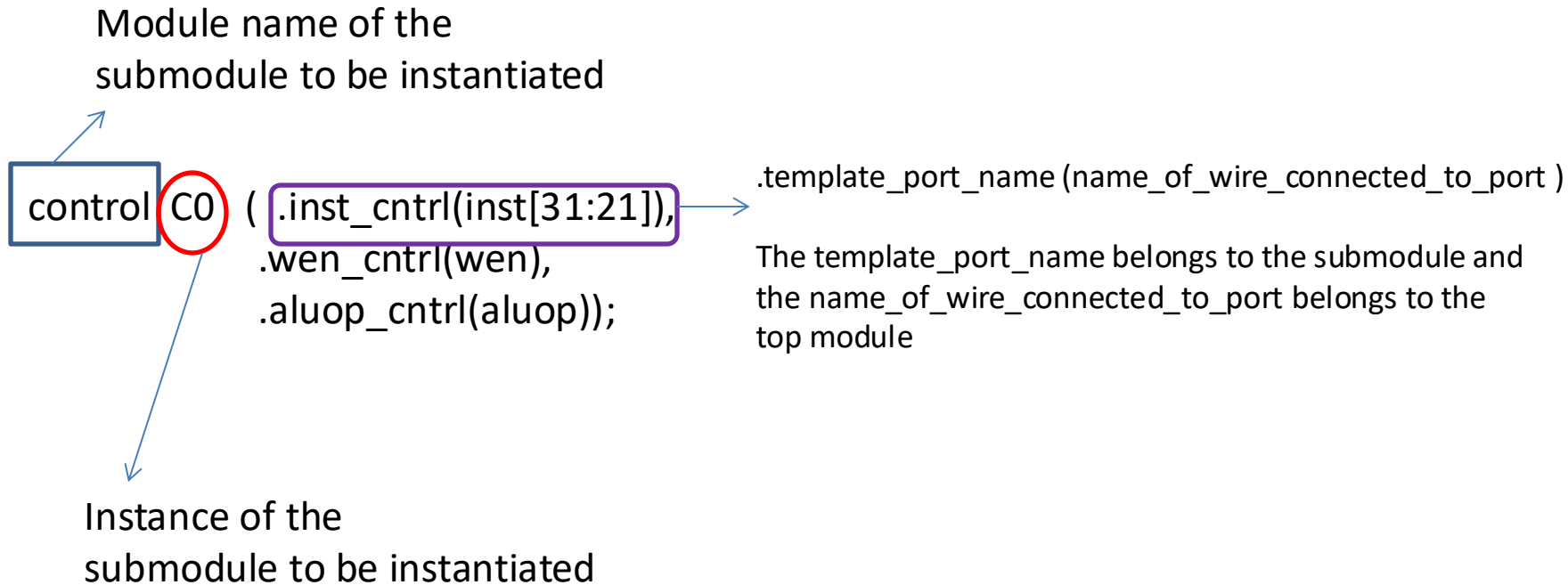

To make the datapath

- You need to instantiate all the following modules and connect them as according to the datapath diagram


control C0

```
(.inst_cntrl(inst[31:21]),.wen_cntrl(wen),.aluop_cntrl(aluop));
```

regfile RF0 (.clk(clk), .rst(rst), .wen(wen), .raddr1(inst[9:5]),
.raddr2(inst[20:16]), .waddr(inst[4:0]), .wdata(aluout),
.rdata1(rdata1), .rdata2(rdata2));

alu ALU0 (.a(rdata1), .b(rdata2), .op(aluop), .out(aluout));

RTL schematic

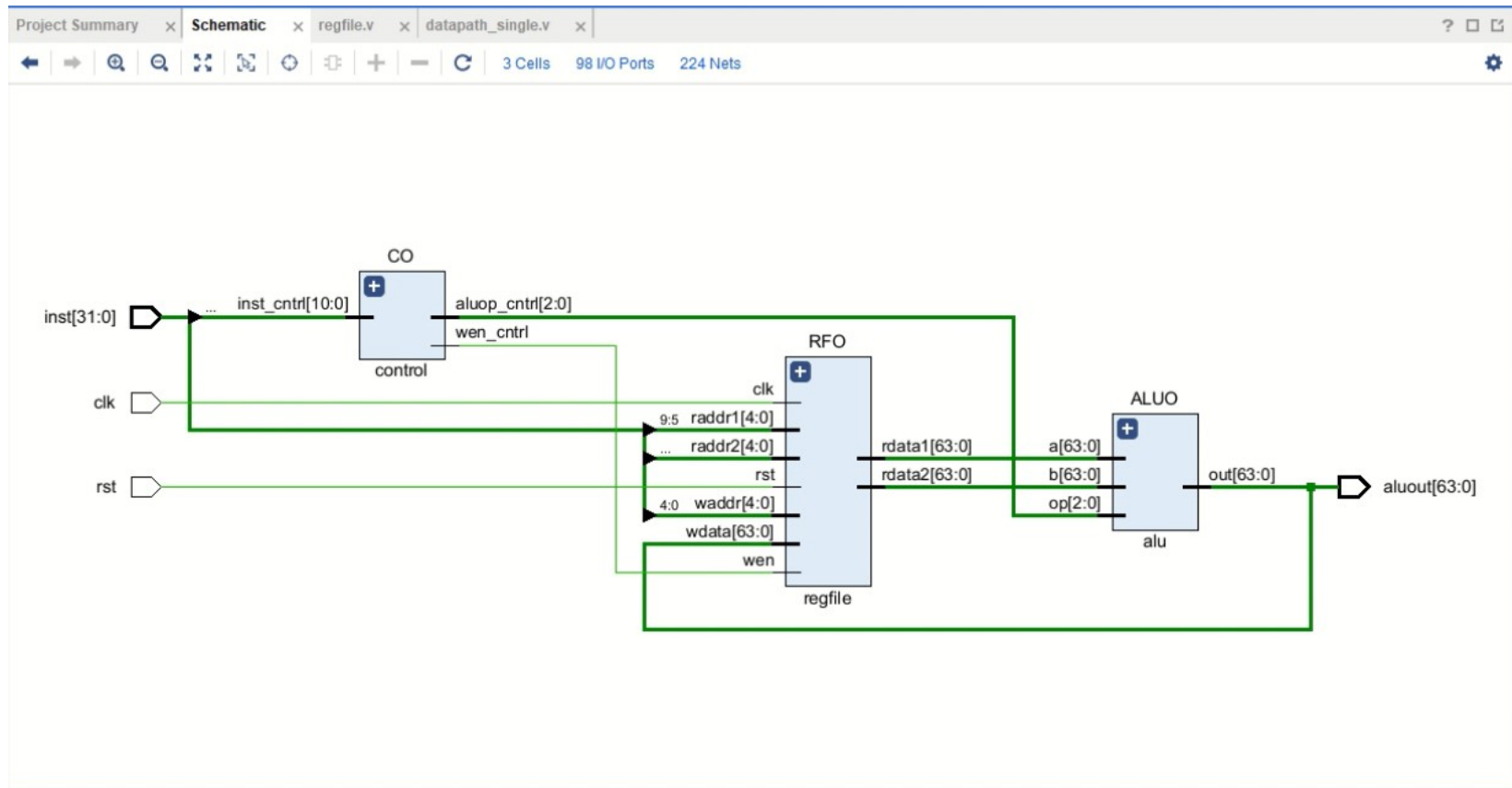

Testing the datapath(change)

- Hardcoded in “regfile.v”

```
regdata[1] <=3
```

```
regdata[2] <=2;
```

Rest all the registers from 0-31 are initialized to zero

Opcode **Rn=source1**

```
inst=32'b000000000000001000000000000100011; // ADD X3, X1, X4
```

Rm=source2 **Rd=dest**

Add X3, X1, X4= [X3] <= [X1] + [X4]

As reg[1] has value 3 and reg 2 has value 0,
the result stored in reg[3] =3